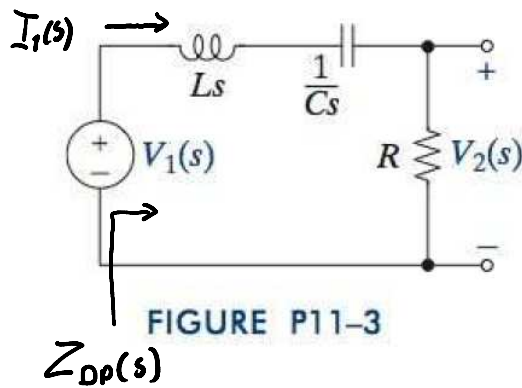


11-3 Find the driving point impedance seen by the voltage source in Figure P11-3 and the voltage transfer function  $T_V(s) = V_2(s)/V_1(s)$ .



$$Z_{op}(s) = \frac{V_1(s)}{I_1(s)}$$

$$T_V(s) = \frac{V_2(s)}{V_1(s)}$$

$$\downarrow I_1(s) = \frac{V_1(s)}{sL + \frac{1}{sC} + R} = \frac{V_1(s) \cdot sC}{s^2LC + sRC + 1}$$

$$\downarrow Z_{op}(s) = \frac{s^2LC + sRC + 1}{sC}$$


---

$$V_2(s) = \frac{V_1(s) \cdot R}{sL + \frac{1}{sC} + R} \Rightarrow T_V(s) = \frac{V_2(s)}{V_1(s)} = \frac{R}{sL + \frac{1}{sC} + R}$$

$$\downarrow T_V(s) = \frac{sRC}{s^2LC + sRC + 1}$$


---

11-7 Find the driving point impedance seen by the voltage source in Figure P11-7 and the voltage transfer function.

$$T_v(s) = V_2(s)/V_1(s).$$

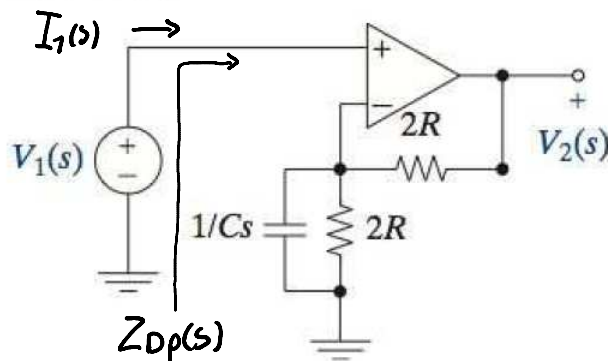


FIGURE P11-7

$$Z_{op}(s) = \frac{V_1(s)}{I_1(s)}$$

$$\bar{I}_1(s) = 0$$

$$\Downarrow$$

$$\underline{\underline{Z_{op}(s) = \infty}}$$

$$Z_{eq}(s) = 2R // \frac{1}{sC} = \left( \frac{1}{2R} + sC \right)^{-1}$$

$$Z_{eq}(s) = \left( \frac{1}{2R} + \frac{s2RC}{2R} \right)^{-1} = \frac{2R}{s2RC + 1}$$

$$T_v(s) = 1 + \frac{2R}{Z_{eq}(s)} = 1 + \frac{2R}{\frac{2R}{s2RC + 1}} = 1 + s2RC + 1$$

$\Downarrow$

$$\underline{\underline{T_v(s) = 2(sRC + 1)}}$$

11-9 Find the voltage transfer function  $T_V(s) = V_2(s)/V_1(s)$  in Figure P11-9.

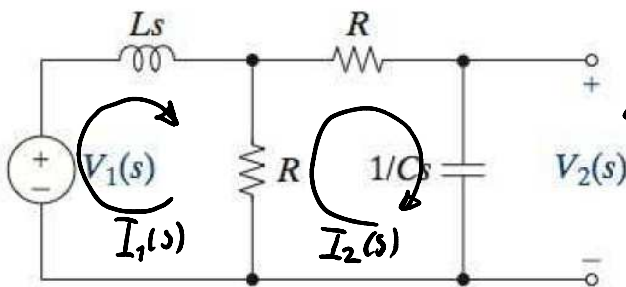


FIGURE P11-9

$$\begin{aligned} 1: I_1(s) \cdot sL + (I_1(s) - I_2(s))R - V_1(s) &= 0 \\ 2: I_2(s) \cdot R + I_2(s) \cdot \frac{1}{sC} + (I_2(s) - I_1(s))R &= 0 \\ 1: (sL + R) \cdot I_1(s) - R \cdot I_2(s) &= V_1(s) \\ 2: -R \cdot I_1(s) + \left(2R + \frac{1}{sC}\right) I_2(s) &= 0 \end{aligned}$$

$$\Downarrow \quad 2: I_1(s) = \frac{2R + \frac{1}{sC}}{R} \cdot I_2(s) = \frac{s2RC + 1}{sRC} \cdot I_2(s)$$

$$1: (sL + R) \frac{(s2RC + 1)}{sRC} \cdot I_2(s) - R \cdot I_2(s) = V_1(s)$$

$$\Downarrow \quad I_2(s) \left( \frac{(sL + R)(s2RC + 1) - sR^2C}{sRC} \right) = V_1(s)$$

$$\Downarrow \quad I_2(s) \left( \frac{s^2 2RLC + sL + s2R^2C + R - sR^2C}{sRC} \right) = V_1(s)$$

$$\Downarrow \quad I_2(s) \left( \frac{s^2 2RLC + s(L + R^2C) + R}{sRC} \right) = V_1(s) \Rightarrow I_2(s) = \frac{V_1(s) \cdot sRC}{s^2 2RLC + s(L + R^2C) + R}$$

$$V_2(s) = I_2(s) \cdot \frac{1}{sC} \Rightarrow V_2(s) = \frac{V_1(s) \cdot R}{s^2 2RLC + s(L + R^2C) + R}$$

$$\Downarrow \quad T_V(s) = \frac{V_2(s)}{V_1(s)} = \frac{R}{s^2 2RLC + s(L + R^2C) + R}$$


---

11-15 Find the voltage transfer function  $T_V(s) = V_2(s)/V_1(s)$  of the cascade connection in Figure P11-15. Locate the poles and zeros of the transfer function.

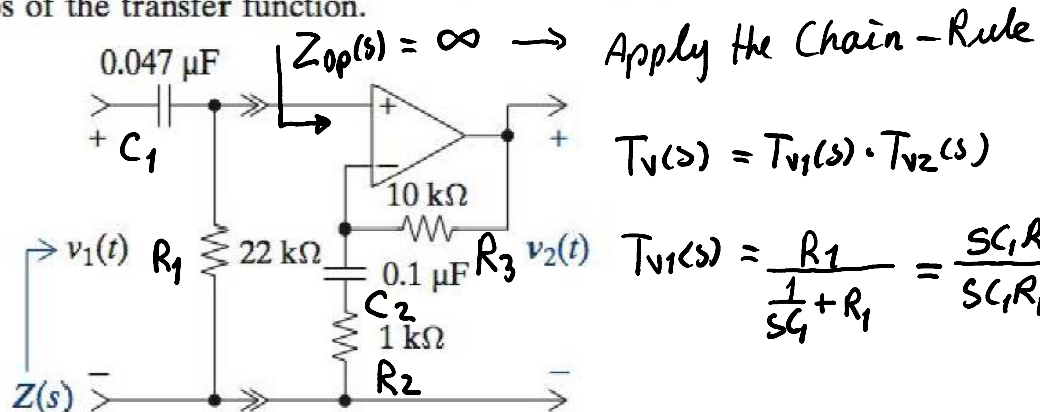


FIGURE P11-15

$$T_{V2}(s) = 1 + \frac{R_3}{\frac{1}{sC_2} + R_2} = 1 + \frac{sC_2 R_3}{sC_2 R_2 + 1} = \frac{sC_2 (R_2 + R_3) + 1}{sC_2 R_2 + 1}$$

$$T_V(s) = \frac{sC_1 R_1}{sC_1 R_1 + 1} \cdot \frac{sC_2 (R_2 + R_3) + 1}{sC_2 R_2 + 1} = \frac{s}{s + \frac{1}{C_1 R_1}} \cdot \frac{C_2 (R_2 + R_3) \cdot (s + \frac{1}{C_2 (R_2 + R_3)})}{C_2 R_2 (s + \frac{1}{C_2 R_2})}$$

$$T_V(s) = \frac{R_2 + R_3}{R_2} \cdot \frac{s \cdot (s + \frac{1}{C_2 (R_2 + R_3)})}{(s + \frac{1}{C_1 R_1}) (s + \frac{1}{C_2 R_2})}$$

$$R_1 = 22 \text{ k}\Omega, R_2 = 1 \text{ k}\Omega, R_3 = 10 \text{ k}\Omega, C_1 = 0.047 \cdot 10^{-6} \text{ F}, C_2 = 0.1 \cdot 10^{-6} \text{ F}$$

$$\frac{1}{C_2 (R_2 + R_3)} = 909.09 \text{ } \pi/\text{s}, \frac{1}{C_1 R_1} = 967.12 \text{ } \pi/\text{s}, \frac{1}{C_2 R_2} = 10000 \text{ } \pi/\text{s}$$

$$\frac{R_2 + R_3}{R_2} = 11$$

$$T_V(s) = 11 \cdot \frac{s (s + 909.09)}{(s + 967.12) (s + 10000)} \rightarrow \text{Zeros: } s = 0, s = -909.09 \text{ } \pi/\text{s}$$

$$\rightarrow \text{Poles: } s = -967.12, s = -10000 \text{ } \pi/\text{s}$$